# **DIGITAL LOGIC DESIGN CEP REPORT (CS-220)**

#### Course Code: CS 220, Course Title: Digital Logic Design Evaluation Rubric

#### Group Members:

Student No.	Name	Roll No.	Batch
51	SYED MUHAMMAD TAIMOOR	CS-031	2020
S2	DANIYAL AMIR	CS-010	2020


CRITERIA AND SCALES								
Criterion 1: To what level has the student understood the problem? [CPA 1]								
0 - 2		3 -	-4	5				
Problem understanding is minimal.		Problem is understo	ood partially	Problem is completely understood				
Criterion 2: To what extent the student implemented the solution? [CPA 1]								
0		1-	-3	4-5				
The solution has not implemented	The solution has not been implemented		omplete. oneous	The solution is complete. Desired outputs have been achieved				
Criterion 3: What le	evel of creativity	is evident in the pr	oposed design? [CI	PA 2]				
0-1		2-	-3	4-5				
No / Poor design		The design is run o	f the mill	The design is innovative				
Criterion 4: What is	Criterion 4: What is the student's level of confidence with the Simulation Tool Interface? [CPA 3]							
0		1-2	3-4		5			
The student is unfamiliar with the tool	The student is fa visible features		The student is fam the unexposed feat the tool		The student is proficient with the tool			
Criterion 5: How w	ell has the studer	nt interconnected th	e circuit componer	its / hardv	vare resources?			
0		1-	-3	4-5				
Student has no idea how to connect the circuit components / hardware resources		Circuit components / hardware resources are not connected properly		Circuit components / hardware resources are properly connected				
Criterion 6: Answe	er to questions re	elated to the design	(Hardware part)					
0	1-2	3-	4	5				
The student did not answer any question	Few questions were answered	The student answer questions	ed most of the	The student answered all the questions				
Criterion 7: Answer to questions related to the design (Simulation Part)								
0		1-4	5-8		9-10			
The student did not answer any question	The student ansi questions	wered a few	The student answered mof the questions		The student answered all the questions			

#### **Unlock Combination Pair Selected:**

As the 1<sup>st</sup> Roll No is 31 and the 2<sup>nd</sup> Roll No is 10, so 31+10=41. According to the Rule, as our least significant digit of 41 is 1, so the Unlock Combination Pairs are:

- 1. 1101
- 2.0110
  - **⊃** In our project, we have used NO OVERLAPPING design.

### **State Diagram:**

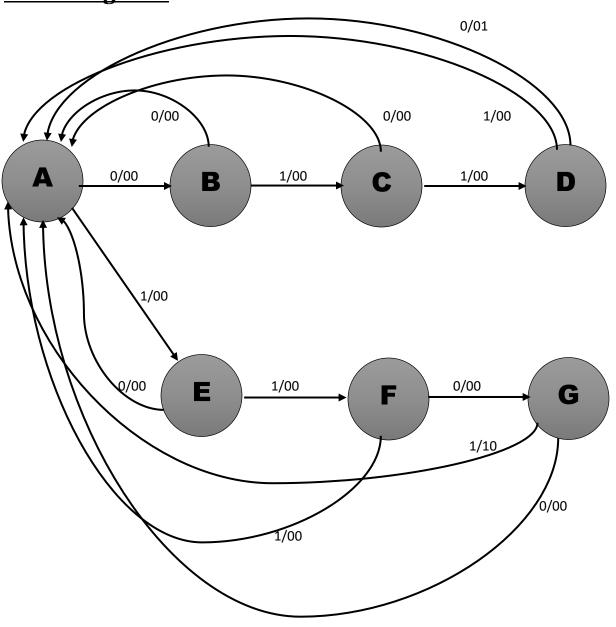

## **State Assignment:**

No. of States = 7

No. of Flipflops needed =  $\left[\overline{Log_2N}\right]$  =  $\left[\overline{Log_27}\right]$  = 3

So, 3 D-FFs will be needed for the design.

A = 000

B = 001

C = 010

D = 011

E = 100


F = 101

G = 110

### **State Minimization:**

	0	1
A	B,00	E,00
В	A,00	C,00
С	A,00	D,00
D	A,01	A,00
E	A,00	F,00
F	G,00	A,00
G	A,00	A,10

### **Pair Implication Chart:**

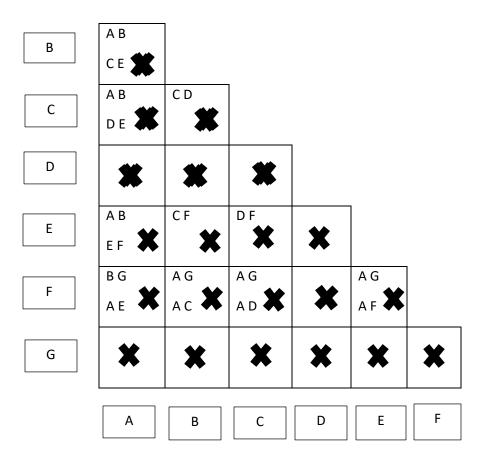


⇒ As no state is compatible to each other, so it is concluded that states will remain same.


## **State Table:**

Present State		Input	Next State			Output		Flipflop Inputs			
Q2(t)	Q1(t)	Q0(t)	Х	Q2(t+1)	Q1(t+1)	Q0(t+1)	Y1	Y0	D2	D1	D0
0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	0	0	0	0
0	0	1	1	0	1	0	0	0	0	1	0
0	1	0	0	0	0	0	0	0	0	0	0
0	1	0	1	0	1	1	0	0	0	1	1
0	1	1	0	0	0	0	0	1	0	0	0
0	1	1	1	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	0
1	0	0	1	1	0	1	0	0	1	0	1
1	0	1	0	1	1	0	0	0	1	1	0
1	0	1	1	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	0	0	1	0	0	0
1	1	1	0	Х	Х	Х	Х	Х	Х	Х	Х
1	1	1	1	Х	Х	Х	Х	Х	Х	Х	Х


## **Deriving Equations:**

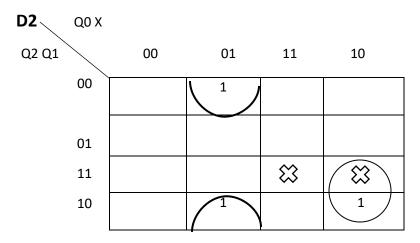


$$D2 = Q1 'Q0' X + Q2 Q0 X'$$

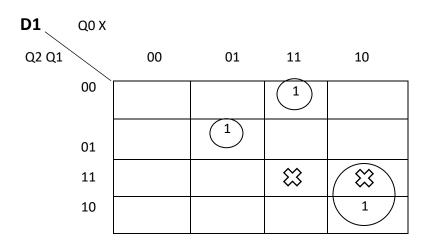

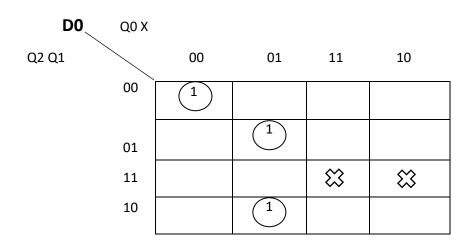
$$D1 = Q2 Q0 X' + Q2' Q1 Q0' X + Q2' Q1' Q0 X$$



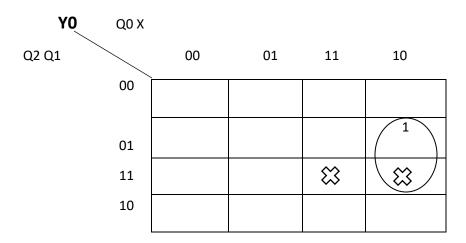D0 = Q2' Q1' Q0' X' + Q2' Q1 Q0' X + Q2 Q1' Q0' X



$$Y0 = Q1 Q0 X'$$

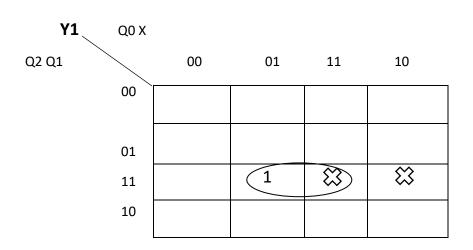

Y1 = Q2 Q1 X

## **Circuit Diagram:**

